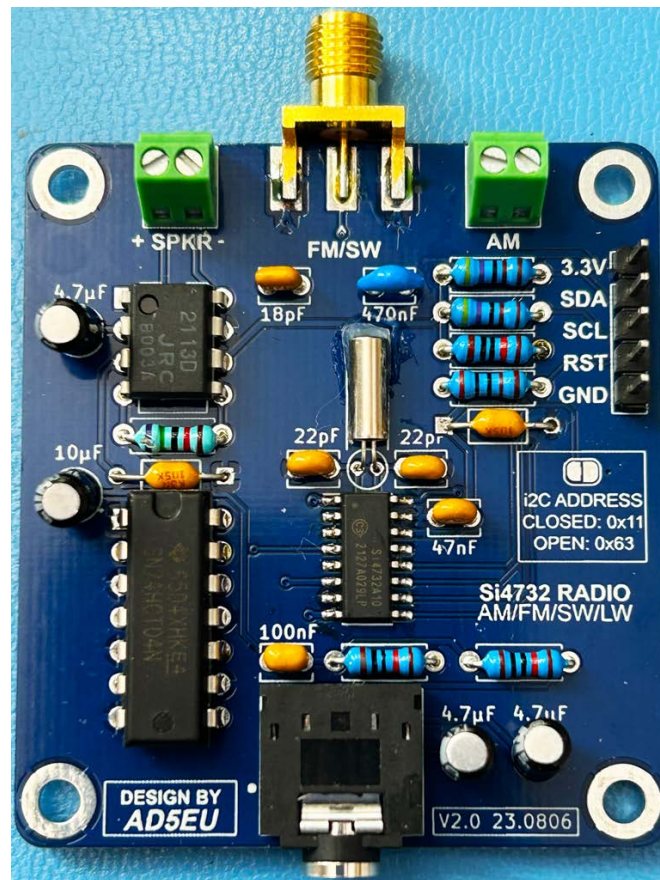


Si4732 Multi-band Radio Through Hole Technology (THT) and Supporting Controller



Developed By
Nancy Gail Daniels
AD5EU

Introduction

The popularity of Skyworks (nee Silicon Labs) based radios has expanded a great deal over the last several years based largely on the excellent core Arduino library developed by Ricardo Lima Caratti. The library (PU2CLR Si4735) is available on github at <https://github.com/pu2clr/SI4735>. Beyond the core library a large number of developers have coded a variety of Arduino applications supporting a variety of displays and user interfaces.

Although there are a number of electronic schematics for radios, radio how to projects (several developed by the author) these tend to rely on surface mount component technology which can be difficult for the casual hobbyist to assemble. Compete radios, such as the ATS25 are available as well.

Given the size of the Facebook group (Si47XX for Radio Experimenters) has grown to nearly 7000 people there is evidently a great deal of interest in radio experimentation. In May 2023 the author was gently challenged to develop a radio which component technology which was more approachable by a broad spectrum of experimenters.


This project proved to be somewhat more difficult than originally expected, not because of the electronic complexity of the radio, which is well understood, but rather from the standpoint of finding "through hole technology" components appropriate for building a full function radio economically. After two iterations a "bullet proof" design was developed along with an Arduino controller/display board. The core radio module can be built in single unit quantities for ~\$20USD excluding the cost of the PCB (available from a variety of suppliers for ~\$5.00USD plus shipping).

A complete radio with display, Arduino controller and controls can be built for approximately double this cost.

Radio Core

The core radio is based on the Si4732 chip. This device internally has the same chip as the Si4735 radio chip, but is in a more hobbyist friendly in a 16 pin SOIC (Small Outline IC) package. This is the only surface mount devices in the radio (through hole packages of the Si473x are not made by Skyworks), but with a relatively large 1.27mm (0.05") pin pitch can be soldered with a little care, and perhaps some form of magnification.

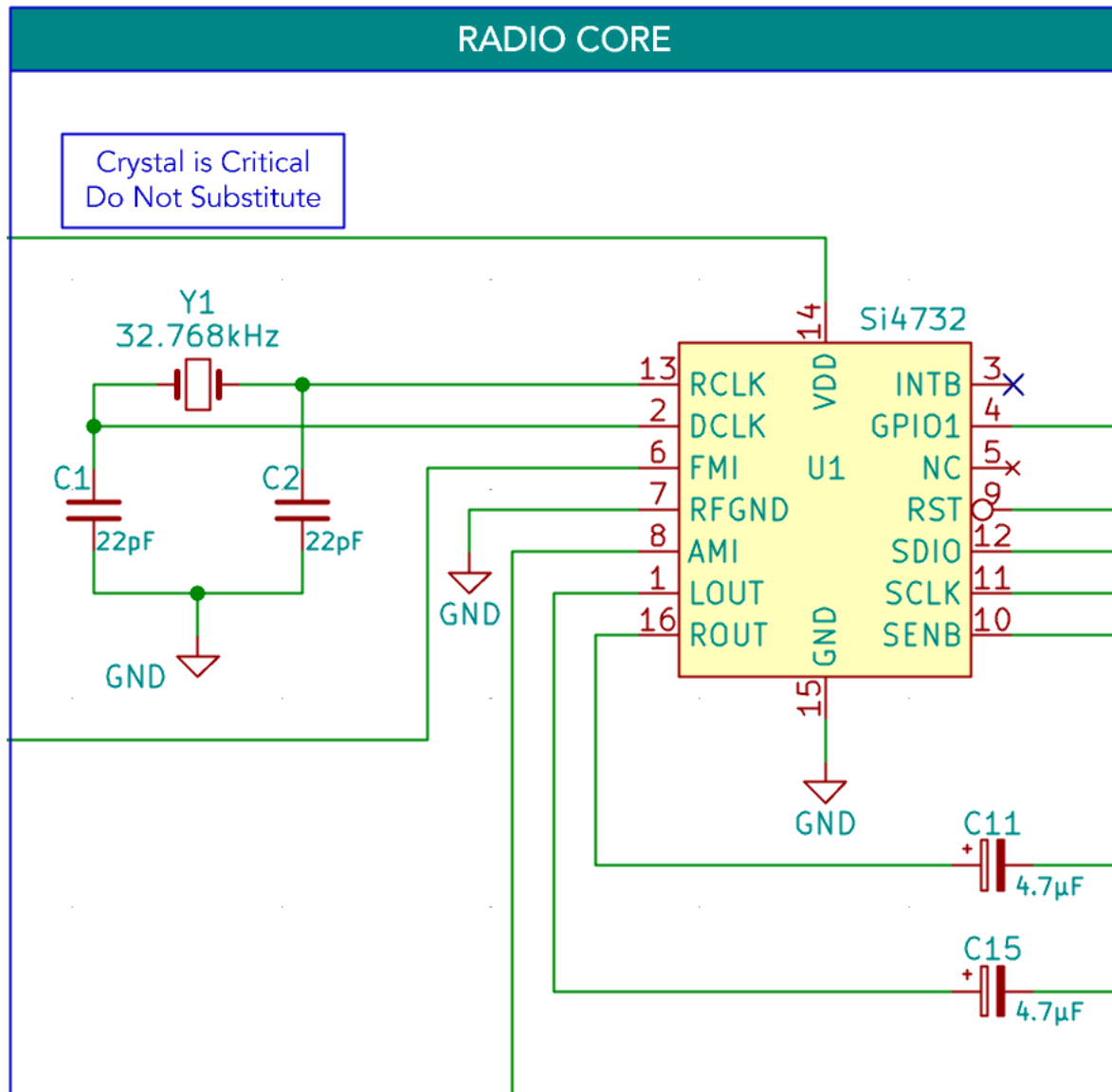The Si4732 chip only requires a few support components – excluding an audio amplifier just nine (9) capacitors and four resistors.



The only critical component (DO NOT SUBSTITUTE) is the 32.768kHz crystal required by the Si473x radio. A number of hobbyists have attempted to build Si473x radios and have had issues making the radio work due to the sensitivity of the radio chip to this component. The recommended crystal is the ECS Inc. ECS-.327-12.5-8X available for ~\$0.50USD. If this crystal is not available to you, ensure that you pick a substitute crystal with the following characteristics:


Load Capacitance: 12.5pf - CRITICAL

Equivalent Series Resistance: 35kΩ - CRITICAL

Tolerance: ±20ppm (tighter tolerance, e.g. ±10ppm acceptable)

Amplifier

The NJM2113 (Japan Radio Corporation) audio amplifier complements the radio. This chip was chosen as it has adequate power for most speakers used in portable radios (0.4W Class AB), is relatively inexpensive (\$1USD), includes internal muting circuitry simplifying the design and is packaged in an easy to assemble 8pin DIP package. The amplifier requires an additional three capacitors, two resistors and a very inexpensive logic chip.

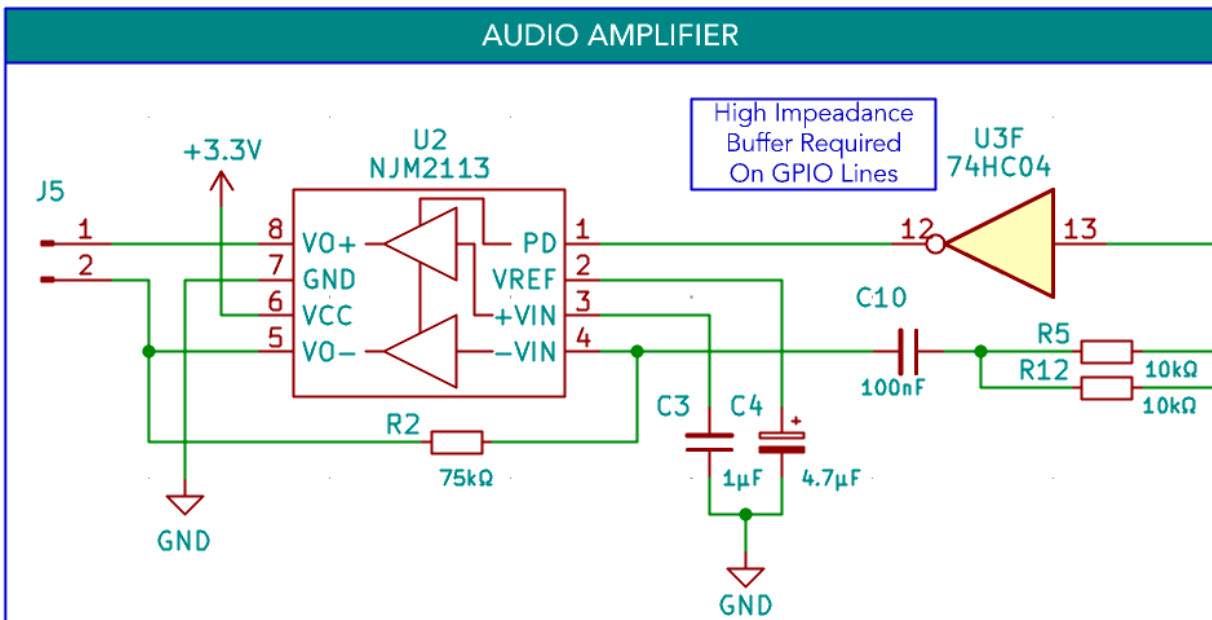


A design feature of this radio is that it uses one of the built in I/O lines of the Si473x chip to control muting saving a pin and I/O pin on the support microcontroller. The I/O lines on the Si473x must not have any electrical loading when the radio boots, or it will hang (not function). A low cost (\$0.20USD) logic chip provides the necessary isolation between the mute circuit of the amplifier and the radio chip. Although the 74HCT04 chip used is relatively large (14 pin DIP package) and only 1/6th of the chip is used, it is the simplest least expensive solution the designer could find.

Complete Radio

The complete radio has a total of 27 components:


12	Capacitors	7	Resistors
1	Crystal	3	Chips (Radio/Amplifier/Logic)
5	External Jacks (FM+SW, AM, Speaker, Headphones, Interface)		

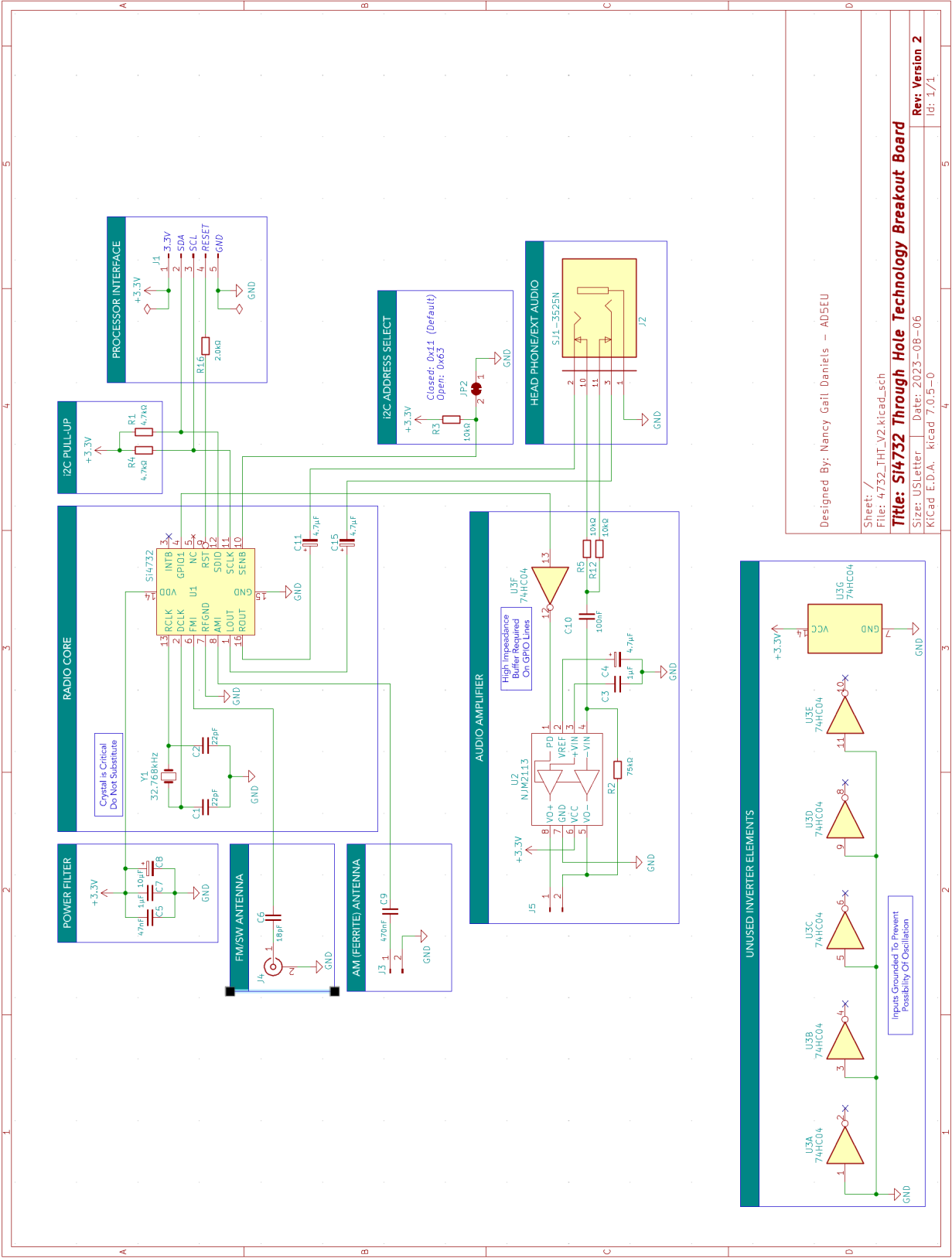The following two pages illustrate the complete schematic and show the bill of materials for the radio.



PCB

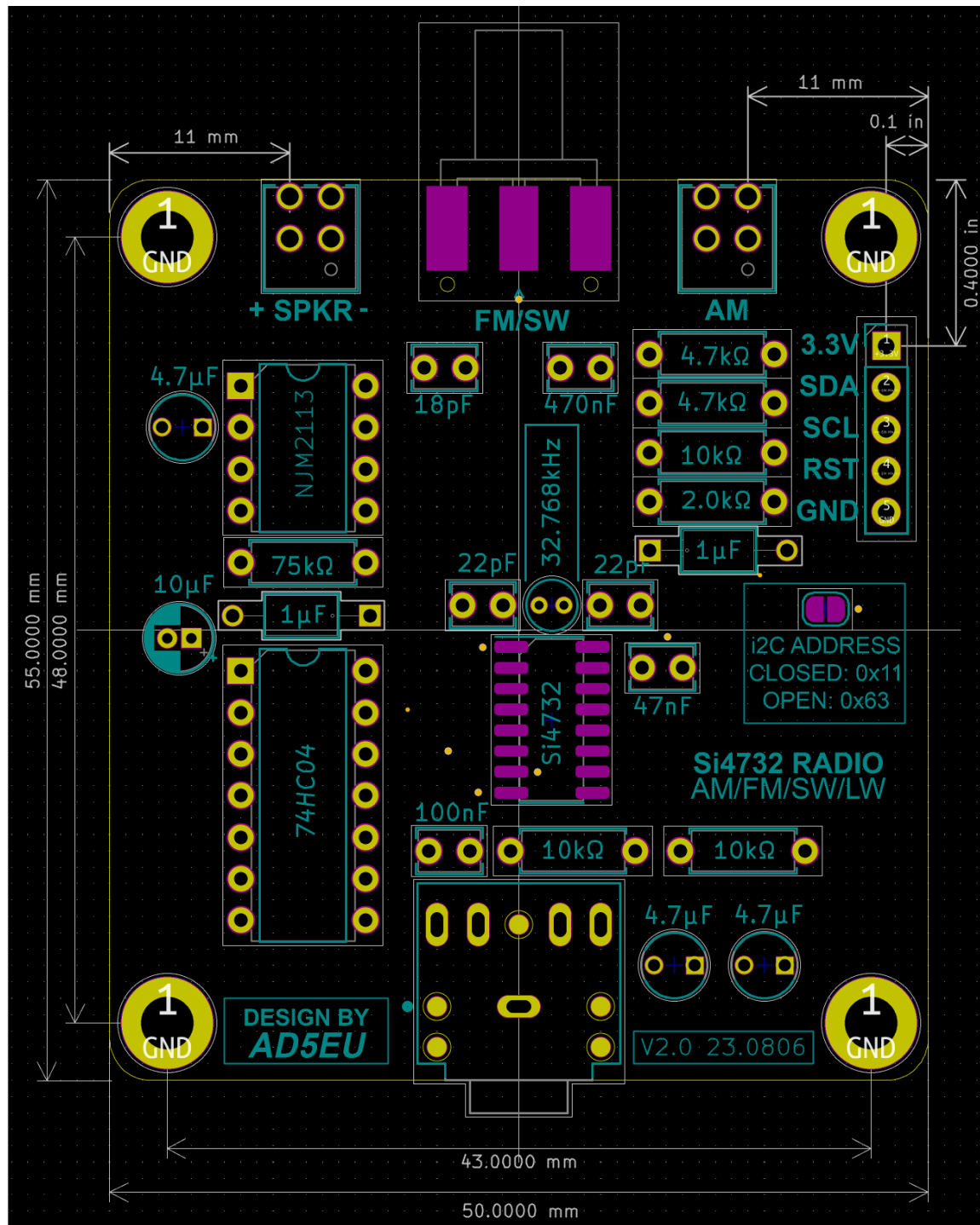The radio is built using a 50mm (1.97") x 55mm (2.16") double sided PCB with M3 (3mm) mounting holes spaced 43mm (1.69") and 46mm (1.81") apart respectively.





Assembly

The radio module can be assembled in less than an hour. The following are the suggested steps for assembling the radio.

Step 1 – The Si4732 chip

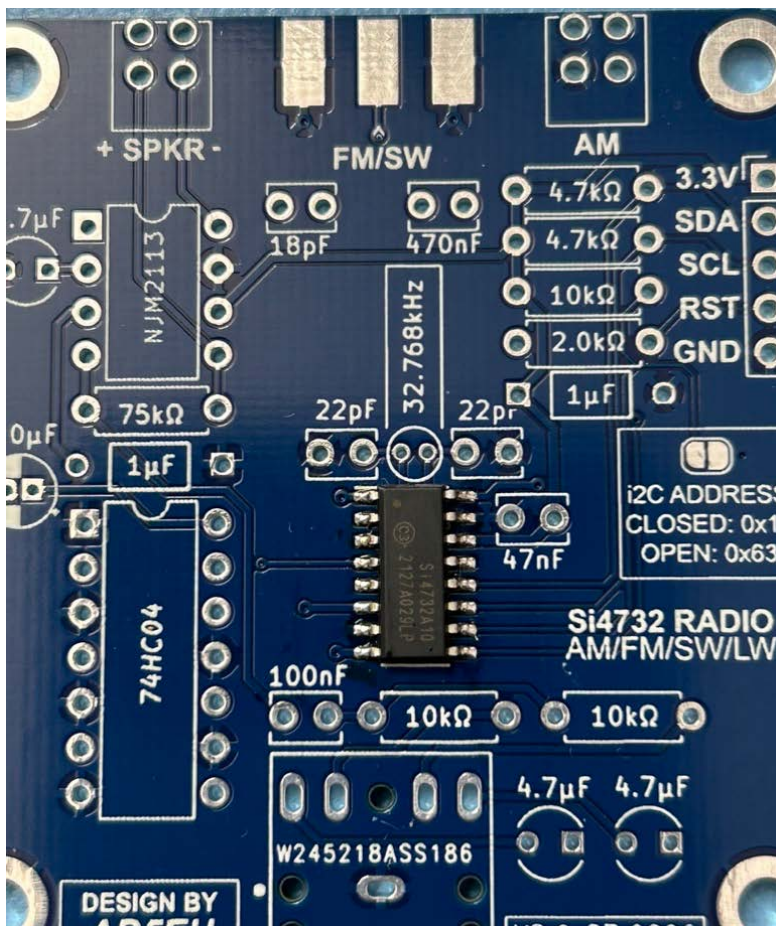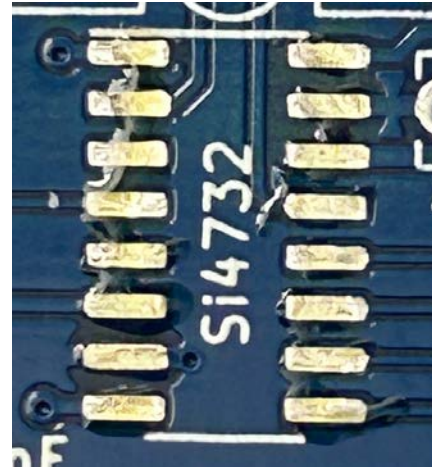The Si4732 is the most difficult part of the board assembly. Although not required, depositing (electronic grade) flux on the Si4732 pads will make soldering the Si4732 easier (shown to the right)




Note the Si4732 chip is sensitive to static electricity and it is recommended that you "ground yourself" while handling the chip to insure it is not damaged.

Step 2 – Resistors

The next step is to solder on the 7 resistors on the board. In the picture below 1% tolerance resistors are used and as such the color coding may be unfamiliar:

Purple Green Black Red	75.0k Ω	Yellow Purple Black Brown	4.70k Ω
Brown Black Black Red	10.0k Ω	Red Black Black Brown	2.00k Ω

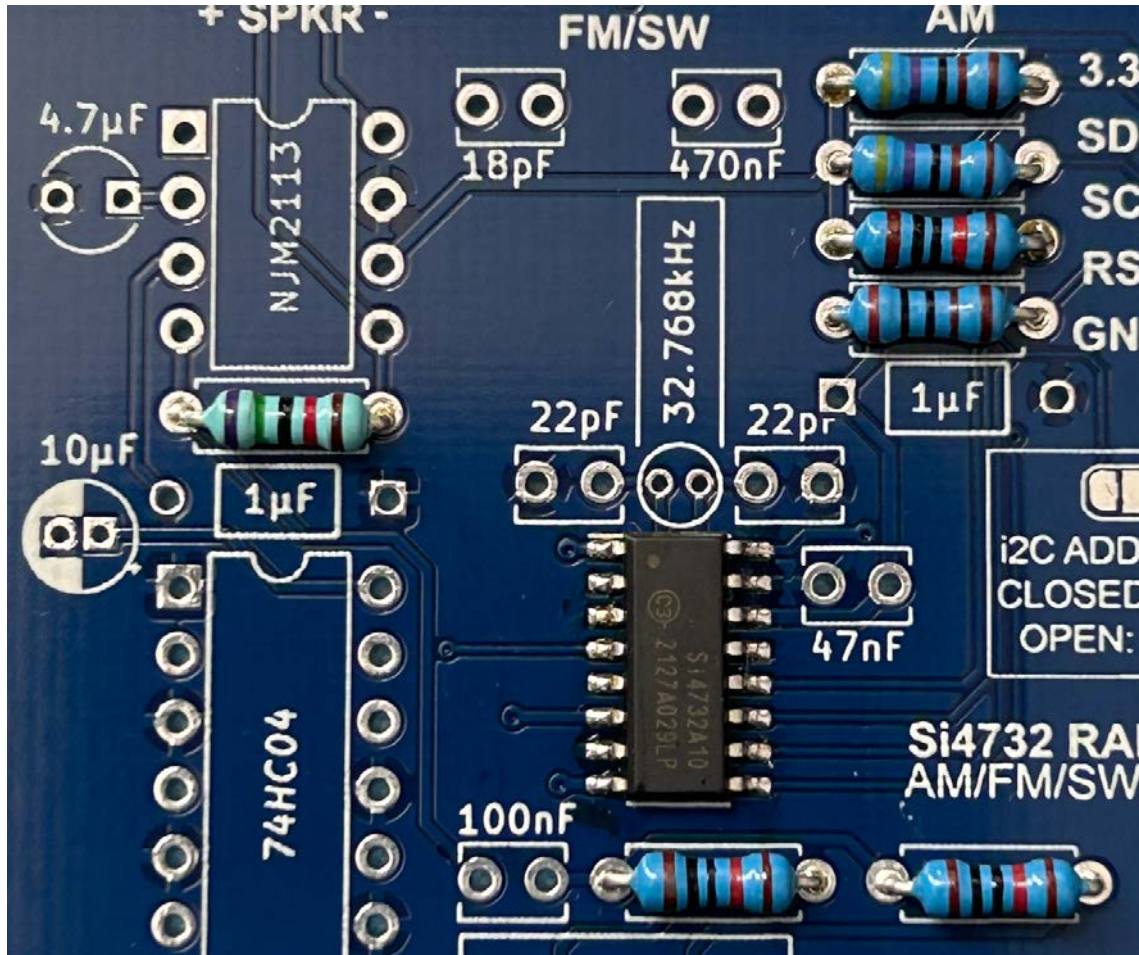


In small quantities 1% resistors can be purchased for the same price as lower tolerance 5% resistors. If you have 5% resistors on hand tolerance is not critical and more commonly available 5% resistors can be used:

Purple Green Orange	75k Ω	Yellow Purple Red	4.7k Ω
Brown Black Orange	10.0k Ω	Red Red Red	2.2k Ω


Step 3 – Small Capacitors

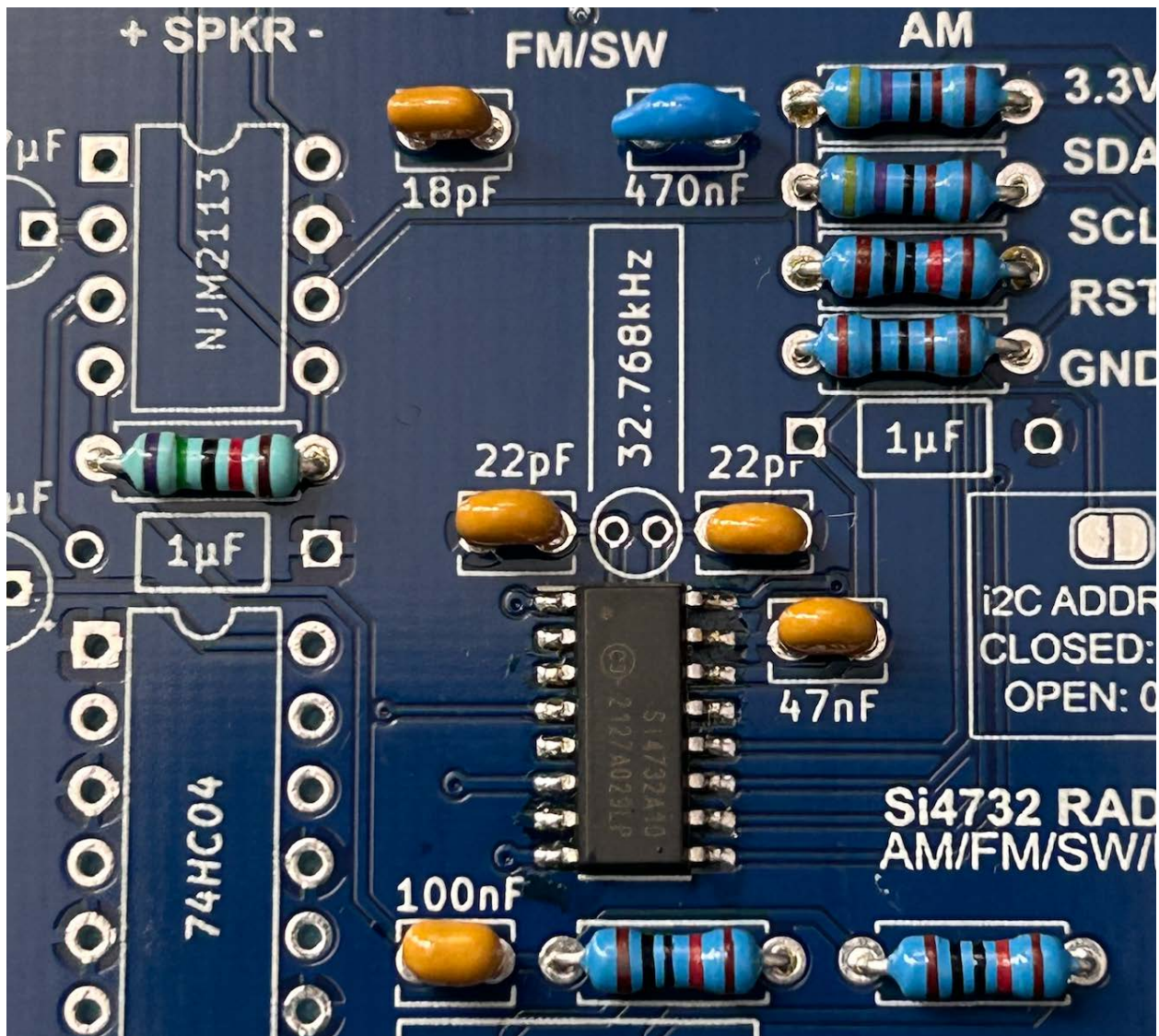Insert and solder the 5 small capacitors. Note that four of the 5 capacitors look exactly the same but differ in value by several orders of magnitude – be very careful not to mix up the capacitors.




Step 4 – Crystal

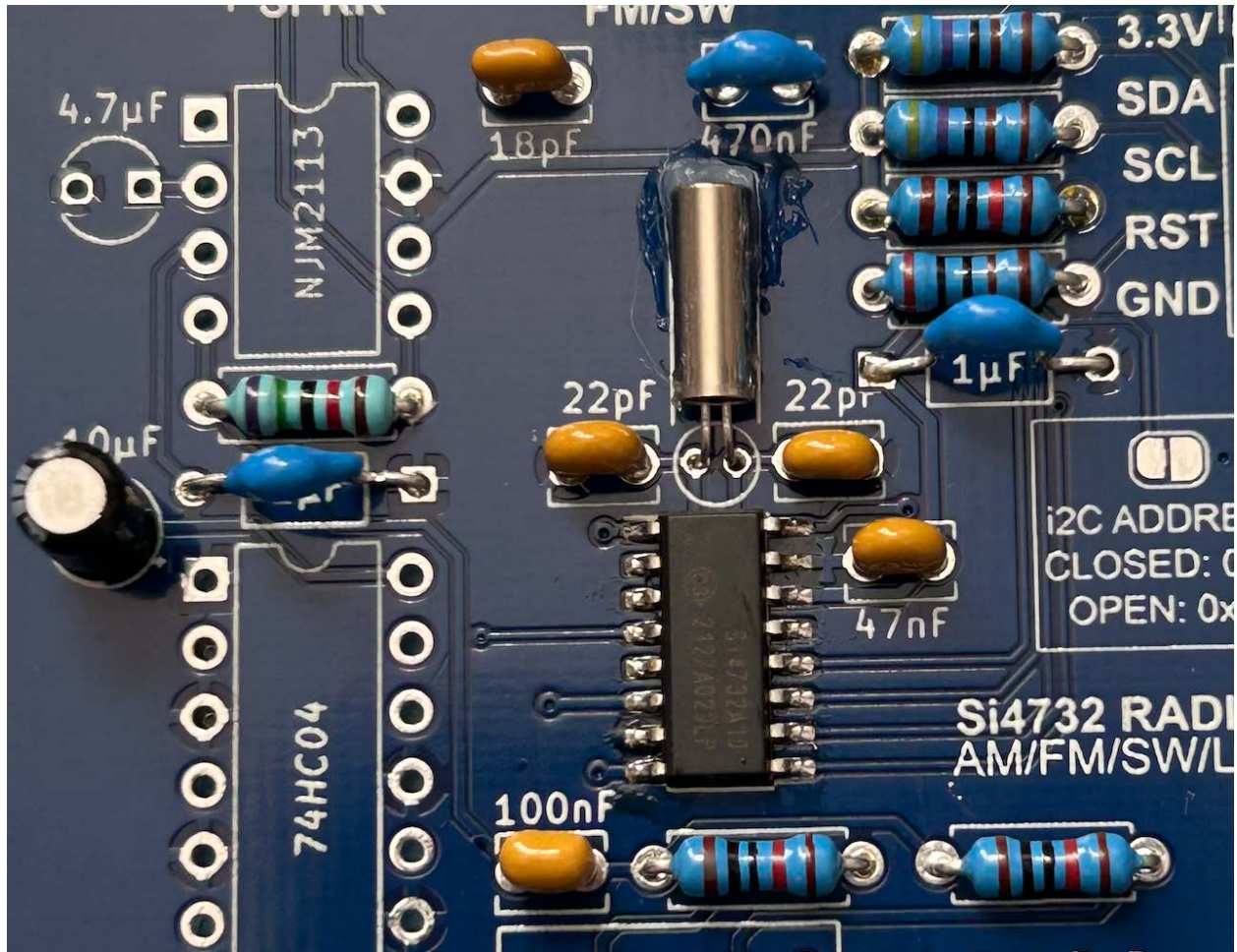Next insert the 32.768kHz crystal. You will notice that the lead spacing on the crystal is quite small and care must be taken when soldering not to accidentally “bridge” solder across the leads. Although not required, a small dab of silicone underneath the crystal will make the radio less susceptible to damage from shock (physically dropping the completed radio).




Step 5 – Large capacitors

Next insert the 6 larger capacitors.

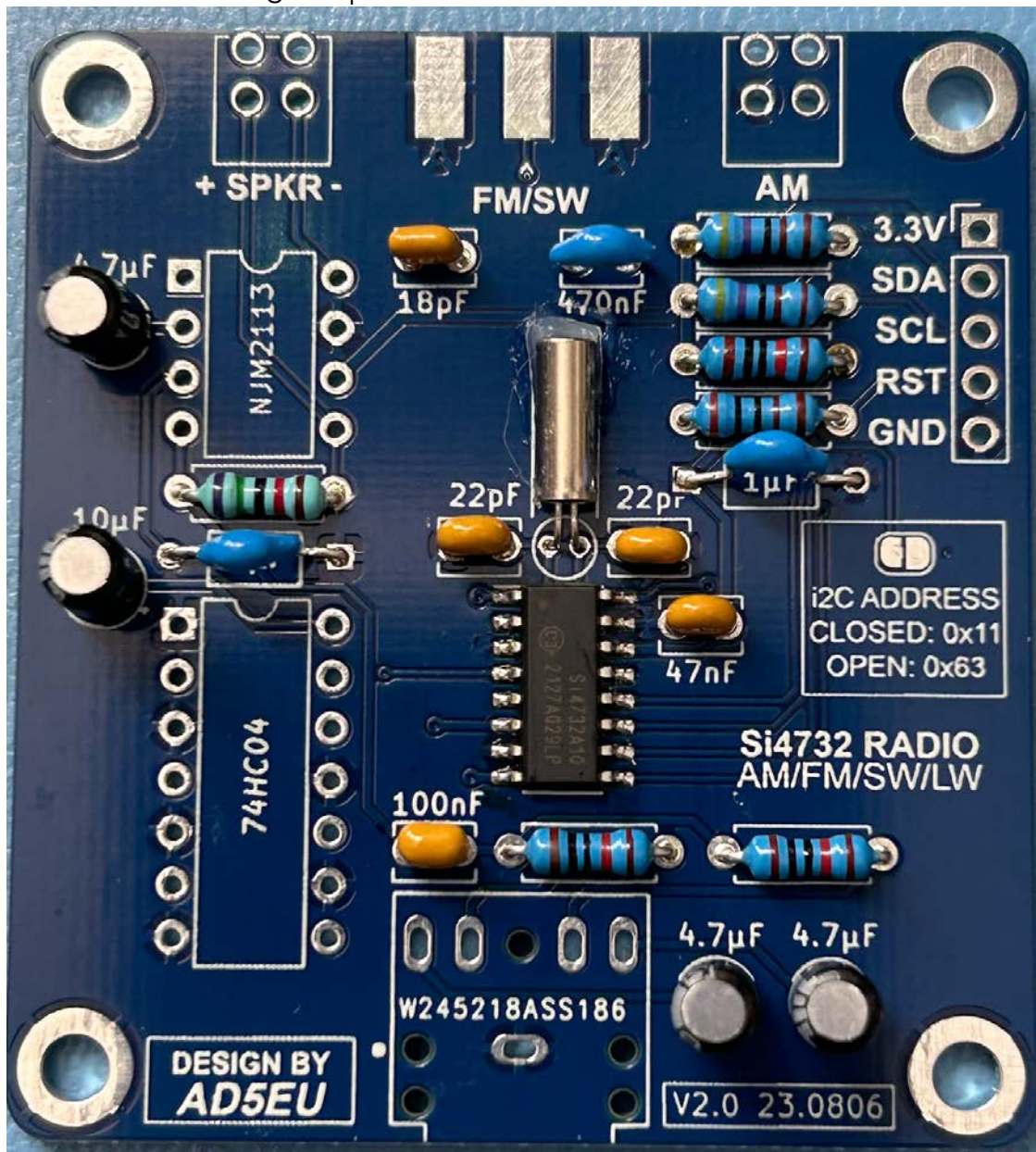

Step 6 – Amplifier and Logic Chip

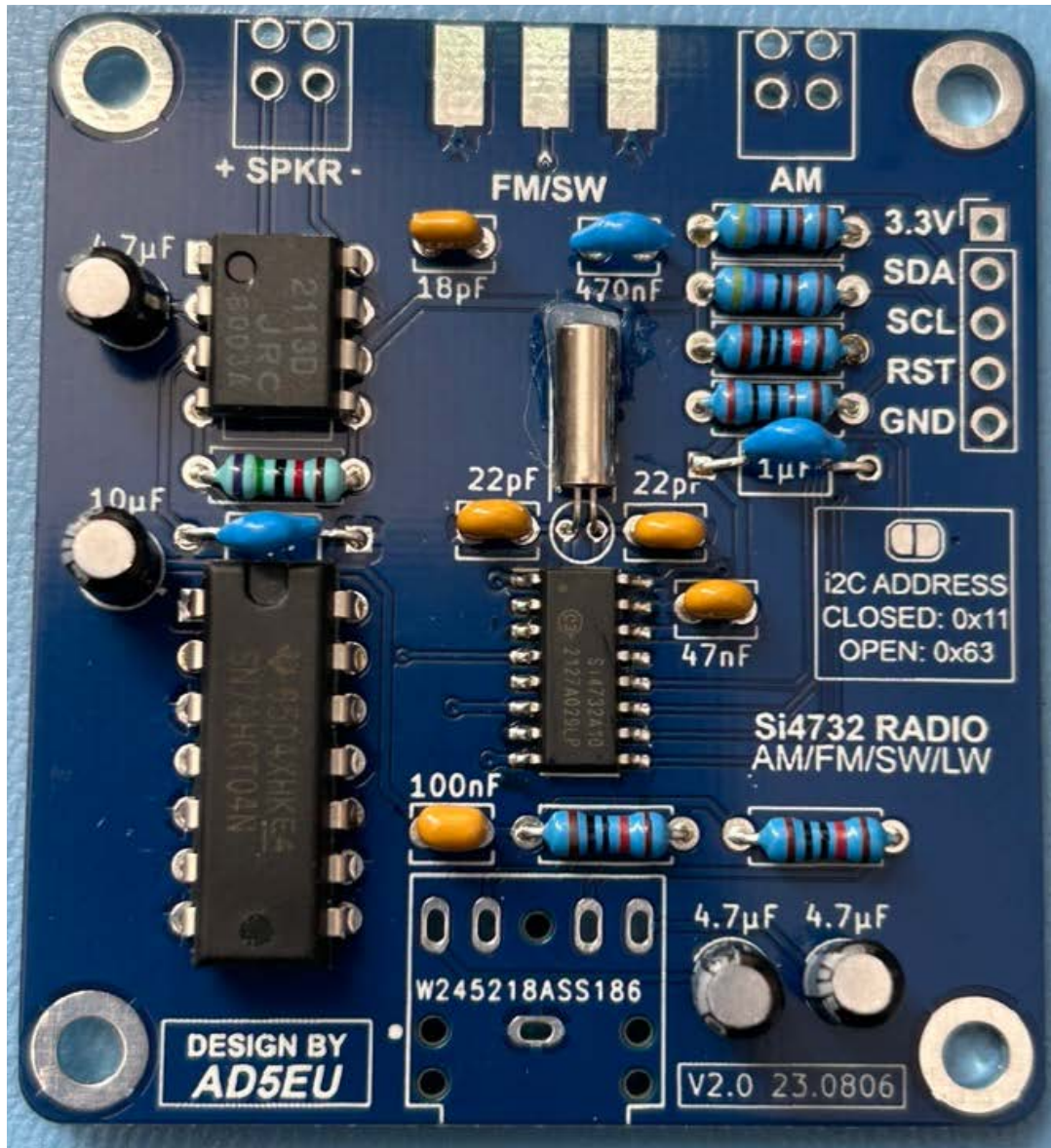Next insert the amplifier (NJM2113) and logic chip (74HCT04). When inserting these chips insure that pin 1 (indicated by the insets/indents on the upper part of the chip) is oriented correctly.



Step 7 – Connectors


The last step before the radio is ready to test is to insert the 5 connectors

SMA jack for Shortwave and FM antenna

Two (2) Terminal blocks for the external speaker and AM antenna

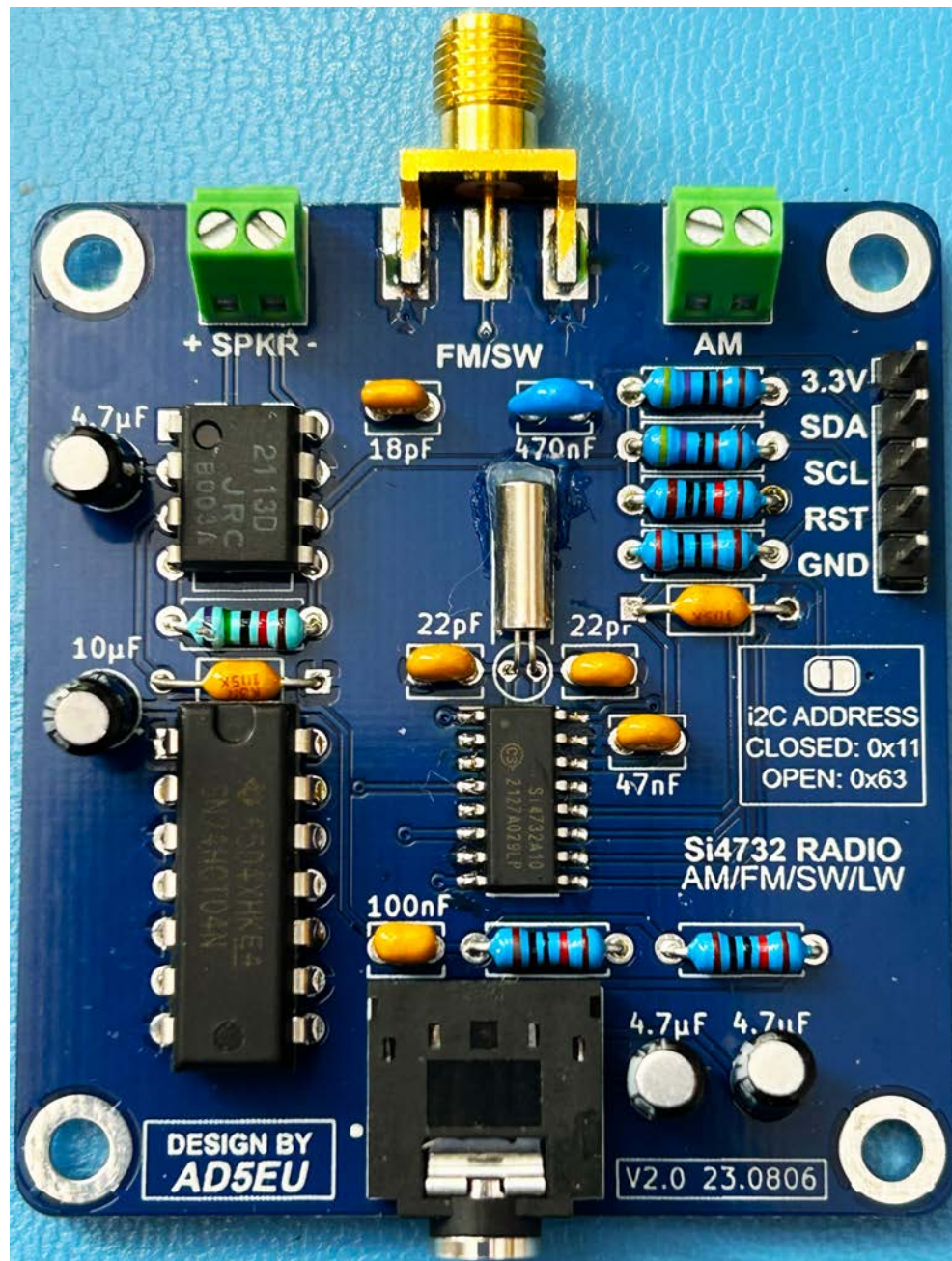3.5mm Audio Jack for Headphones

5 pin) 0.1 header pins for connection to the Arduino



Testing

To test the radio, the 5 pin connector needs to be connected to your Arduino. The key when pairing the radio with an Arduino is that the Si4732 radio board requires 3.3V and does not have any on board voltage regulator. It is therefore recommended that legacy 5V Arduino boards are NOT used with the board.

One of the least expensive and capable Arduino variants is based on the Raspberry Pi RP2040. Although the following is based on the Adafruit Feather RP2040 any of the RP2040 Arduino variants can be used. Only 5 connections are required.

